
Electric circuits

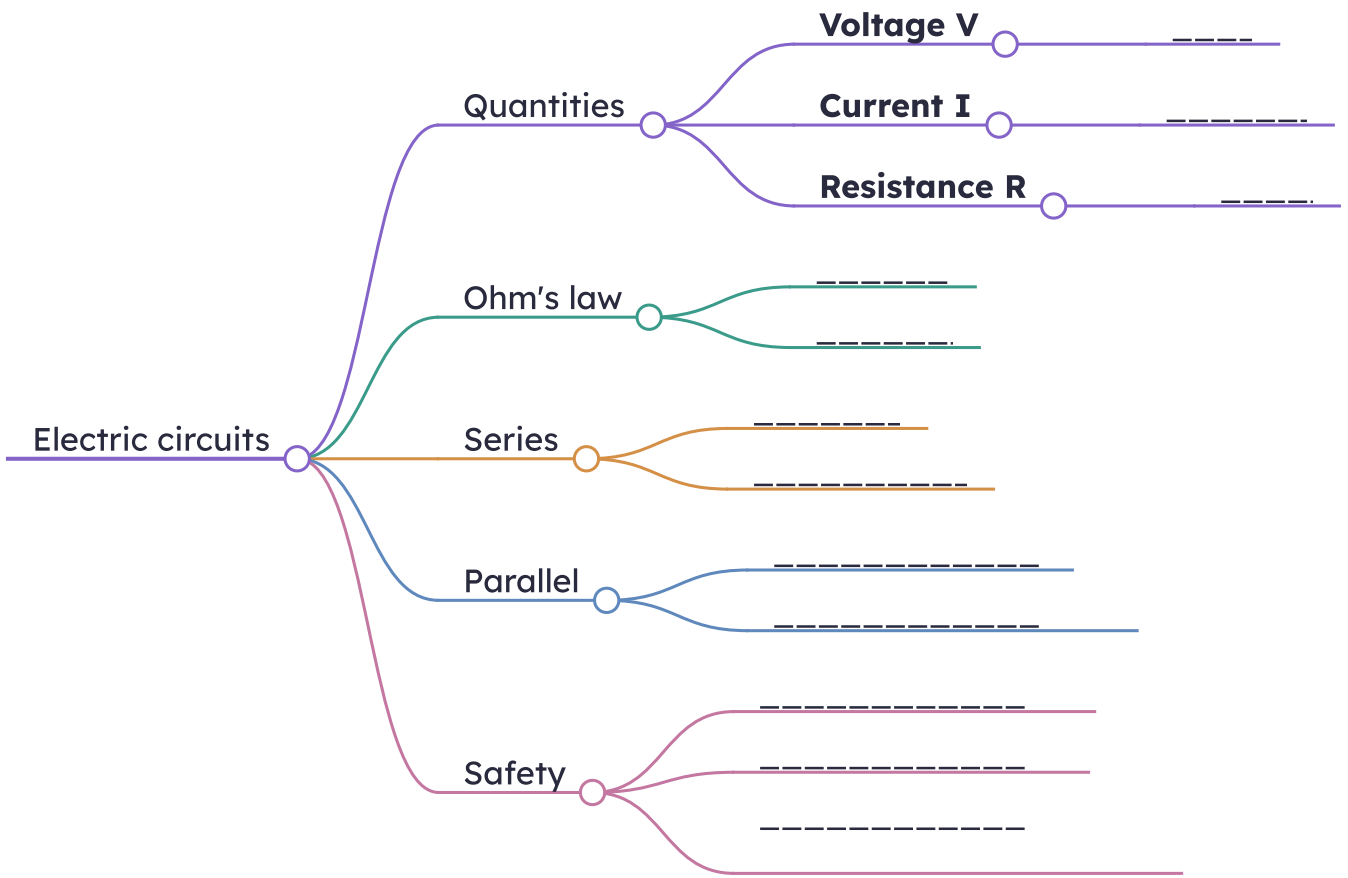
Fill the branches with key terms and explanations from memory. Compare with the answer key on the next page.



Name _____ Date _____

Electric circuits

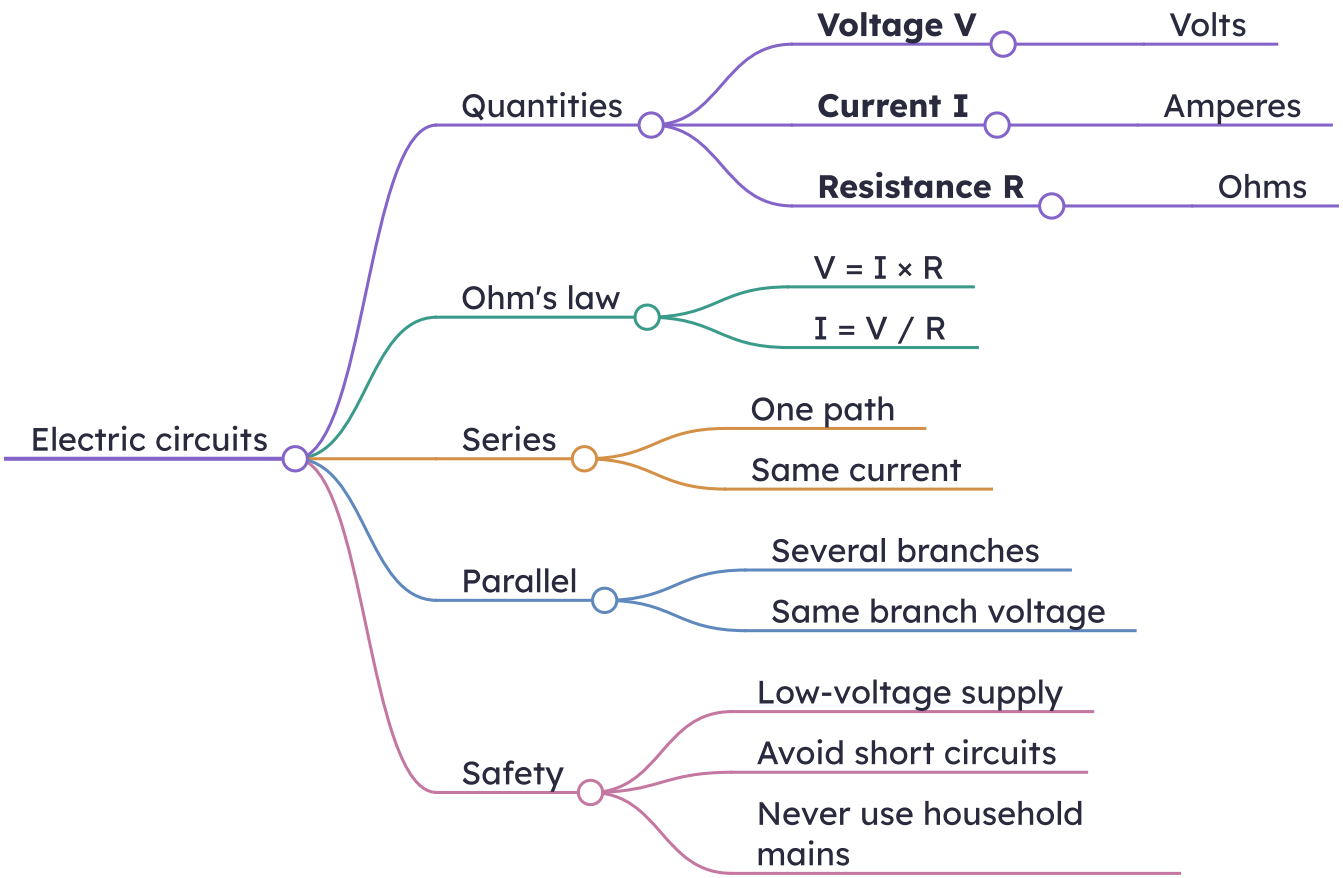Distinguish current, voltage, resistance, and circuit arrangement.



Read one branch at a time. Then cover the details and explain them in your own words.